
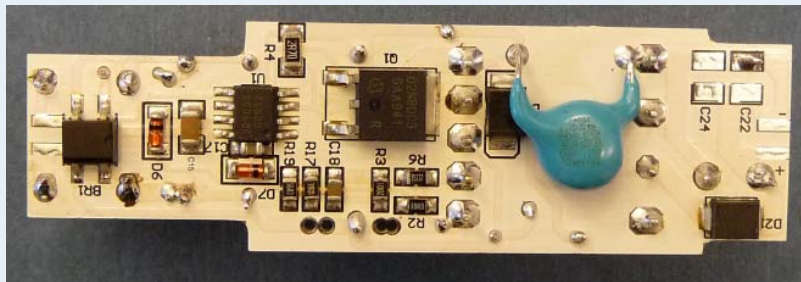
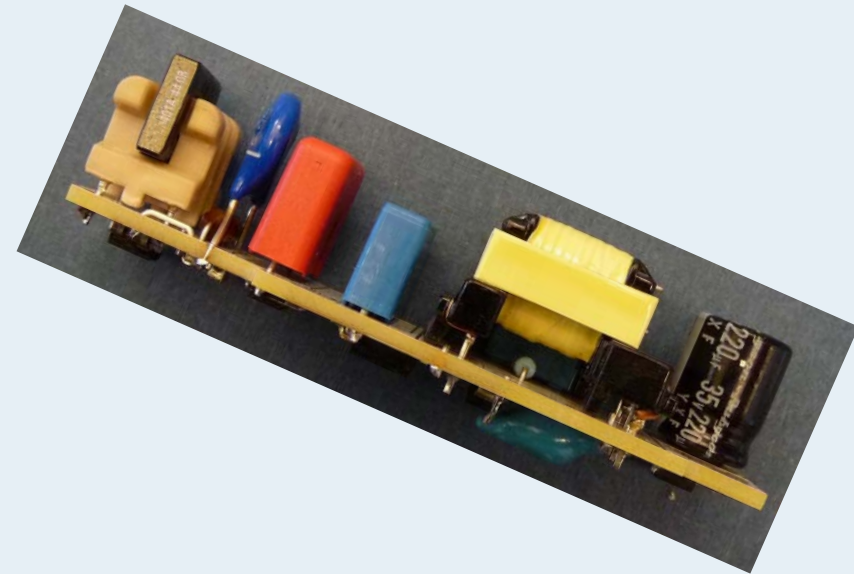


Ali Fawaz  
Senior Application  
Engineer

# POWER FACTOR CORRECTION

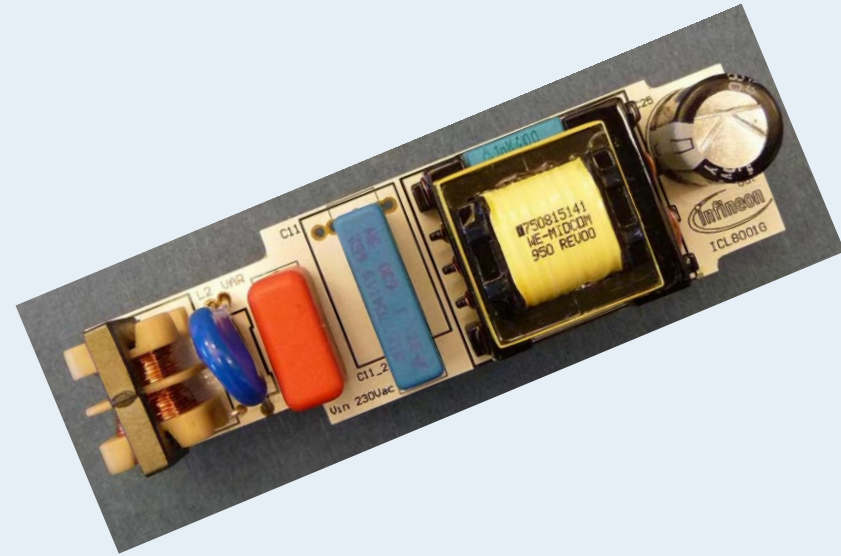

Never stop thinking

# Infineon's Rankings



Power	Industrial	Chip Card	Auto- motive
# 1	# 1	# 1	# 1
Market share 10%	Market share 8%	Market share 26%	Market share 9%
IMS Research, July 2009	Semicast, May 2008	Frost & Sullivan, October 2009	Strategy Analytics, July 2009

Power Factor basics

Definition of Power factor

PF for various loads

Total Harmonic Distortion

PF correction methods

ICL8001G: High PFC Dimmable LED Driver

## Power Factor basics

Definition of Power factor

PF for various loads

Total Harmonic Distortion

PF correction methods

ICL8001G: High PFC Dimmable LED Driver

# What is Power Factor? Why is it important for lighting?



## **Power Factor is a measure of how effectively the load takes power from the line (power plant)**

→ Alternate definition: PF provides a measure of how close your load is to a incandescent light bulb (which has a PF of 1)

❑ **Systems with Low PF require additional power to be generated by utilities**

❑ **Lighting consumes ~20% of all generated power.**

❑ **Much of this power is consumed by traditional bulbs with PF of 1**

❑ **Transition to low PF LED bulbs negates some of these savings.**

→ **High power factor solutions are required for LED bulbs and fixtures**

# Power Factor Requirements -- Regulatory

- **DOE energy star requires PF >0.7 for energy star rating of LED light sources**
- **Europe EN61000-3-2 requires power factor to meet harmonic requirements for light sources above 25W**

**These standards provide a baseline requirements!**

**→ Market requirements for LED bulbs and fixtures are driving PF >0.9 for powers as low as 5W.**

# Detailed of Low Power factor effects

- **A Power Factor less than 1 could result in the problems below**
  
- Power is recycled from the LED Bulb/ Fixture to the power source?
  
- Harmonics from LED bulb/ fixture are degrading the line and affecting the performance of other equipment on the line
  
- The load is generating additional losses
  
- The load is requiring that the power grid provide more power than used.

Power Factor basics

Definition of Power factor

PF for various loads

Total Harmonic Distortion


PF correction methods

ICL8001G: High PFC Dimmable LED Driver
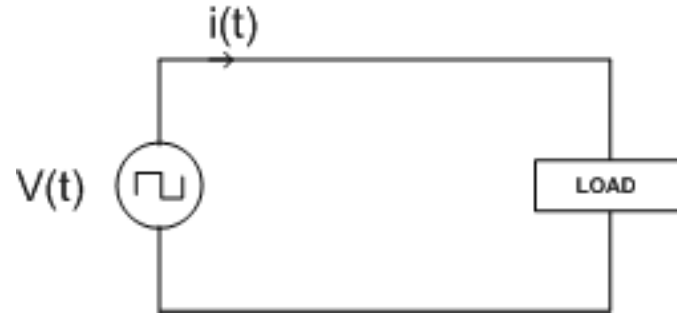
# Definition of Power Factor

- Power Factor is defined as

$$P.F = \frac{\text{AVERAGE POWER}}{\text{APPARENT POWER}}$$



- Derivation of Average Power

$$P_{\text{avg}} = \frac{1}{T} \cdot \int_0^T p(t) dt = \frac{1}{T} \cdot \int_0^T v(t) \cdot i(t) dt$$

A periodic voltage  $v(t)$  can be expressed in Fourier Series as:

$$v(t) = V_{\text{dc}} + \sum_{k=1}^{\infty} \left( V_k \cdot \sin \left( \omega t + \theta_k \right) \right)$$

# Average Power

For Pure AC voltages  $V_{dc}=0$

$$v(t) = \sum_{k=1}^{\infty} (V_k \cdot \sin(k\omega t + \theta_k)) = V_1 \cdot \sin(\omega t + \theta_1) + V_2 \cdot \sin(2\omega t + \theta_2) + V_3 \cdot \sin(3\omega t + \theta_3) + \dots$$

Similarly a current  $i(t)$  that is periodic can be represented as:

$$\sum_{r=1}^{\infty} (I_r \cdot \sin(r\omega t + \phi_r)) = I_1 \cdot \sin(\omega t + \phi_1) + I_2 \cdot \sin(2\omega t + \phi_2) + I_3 \cdot \sin(3\omega t + \phi_3) + \dots$$

$$P_{avg} = \frac{1}{T} \cdot \int_0^T p(t) dt = \frac{1}{T} \cdot \int_0^T v(t) \cdot i(t) dt$$

# Average Power

$$P_{\text{avg}} = \frac{1}{T} \cdot \int_0^T V_1 \cdot \sin(\omega t + \theta_1) \cdot (I_1 \cdot \sin(\omega t + \phi_1)) + V_2 \cdot \sin(2\omega t + \theta_2) \cdot (I_2 \cdot \sin(2\omega t + \phi_2)) + V_3 \cdot \sin(3\omega t + \theta_3) \cdot (I_3 \cdot \sin(3\omega t + \phi_3)) + \dots dt$$

+

$$\frac{1}{T} \cdot \int_0^T V_1 \cdot \sin(\omega t + \theta_1) \cdot I_2 \cdot \sin(2\omega t + \phi_2) + V_1 \cdot \sin(\omega t + \theta_1) \cdot I_3 \cdot \sin(3\omega t + \phi_3) + V_1 \cdot \sin(\omega t + \theta_1) \cdot I_4 \cdot \sin(4\omega t + \phi_4) + \dots dt$$



Unlike Terms (different frequencies)  $r \neq k$ ;  
 deliver zero Average Power. Therefore,

$$P_{\text{avg}} = \frac{1}{T} \cdot \int_0^T \sum_{k=1}^{\infty} (V_k \cdot I_k \cdot \sin(k\omega t + \theta_k) \cdot \sin(k\omega t + \phi_k)) dt$$

# Average Power

$$P_{\text{avg}} = \sum_{k=1}^{\infty} \left( \frac{V_k \cdot I_k}{2} \cdot \cos(\theta_k - \phi_k) \right) \quad \text{In terms of Peak Voltage and Peak Current}$$

$$P_{\text{avg}} = \sum_{k=1}^{\infty} \left( V_{\text{rms}k} \cdot I_{\text{rms}k} \cdot \cos(\theta_k - \phi_k) \right) \quad \text{In terms of RMS voltage and RMS current}$$


## ■ P.F Formulas

$$P \cdot F = \frac{\sum_{k=1}^{\infty} \left( V_{\text{rms}k} \cdot I_{\text{rms}k} \cdot \cos(\theta_k - \phi_k) \right)}{V_{\text{rms}} \cdot I_{\text{rms}}} \quad \text{P.F Mother Equation}$$
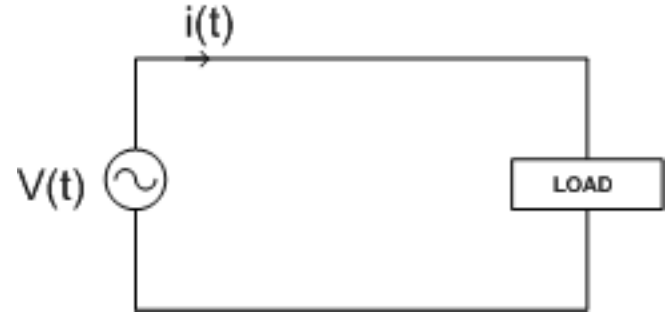
# Power Factor Formulas

- Assuming  $V(t)$  is an ideal sinusoidal voltage Source:

$$P \cdot F = \frac{V_{rms1} \cdot I_{rms1}}{V_{rms} \cdot I_{rms}} \cdot \cos(\theta_1 - \phi_1)$$



$$P \cdot F = \frac{I_{rms1}}{I_{rms}} \cdot \cos(\theta_1 - \phi_1) = K_{disp} \cdot K_{dist}$$

$$K_{dist} = \frac{I_{rms1}}{I_{rms}} \quad \text{Distortion Factor}$$

$$K_{disp} = \cos(\theta_1 - \phi_1) \quad \text{Displacement Factor}$$

$\theta_1 - \phi_1$  Displacement angle between  $V(t)$  and  $i(t)$  at Fundamental frequency.

Power Factor basics

Definition of Power factor

PF for various loads


Total Harmonic Distortion

PF correction methods


ICL8001G: High PFC Dimmable LED Driver
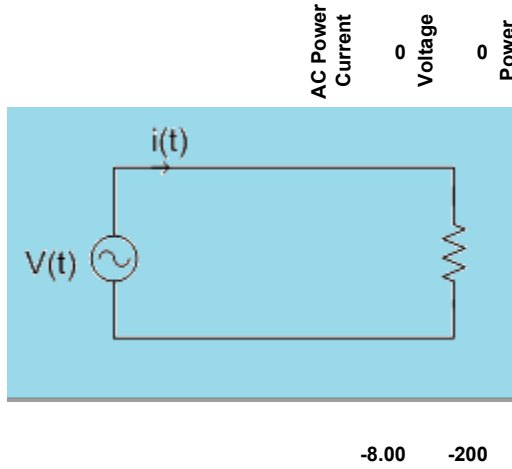
# AC Power at PF = 1 Resistive Load (Incandescent Light Bulb)

There is no phase shift between Voltage and Current.  
All power taken from the source is used by load




1 voltage 2 current 3 power

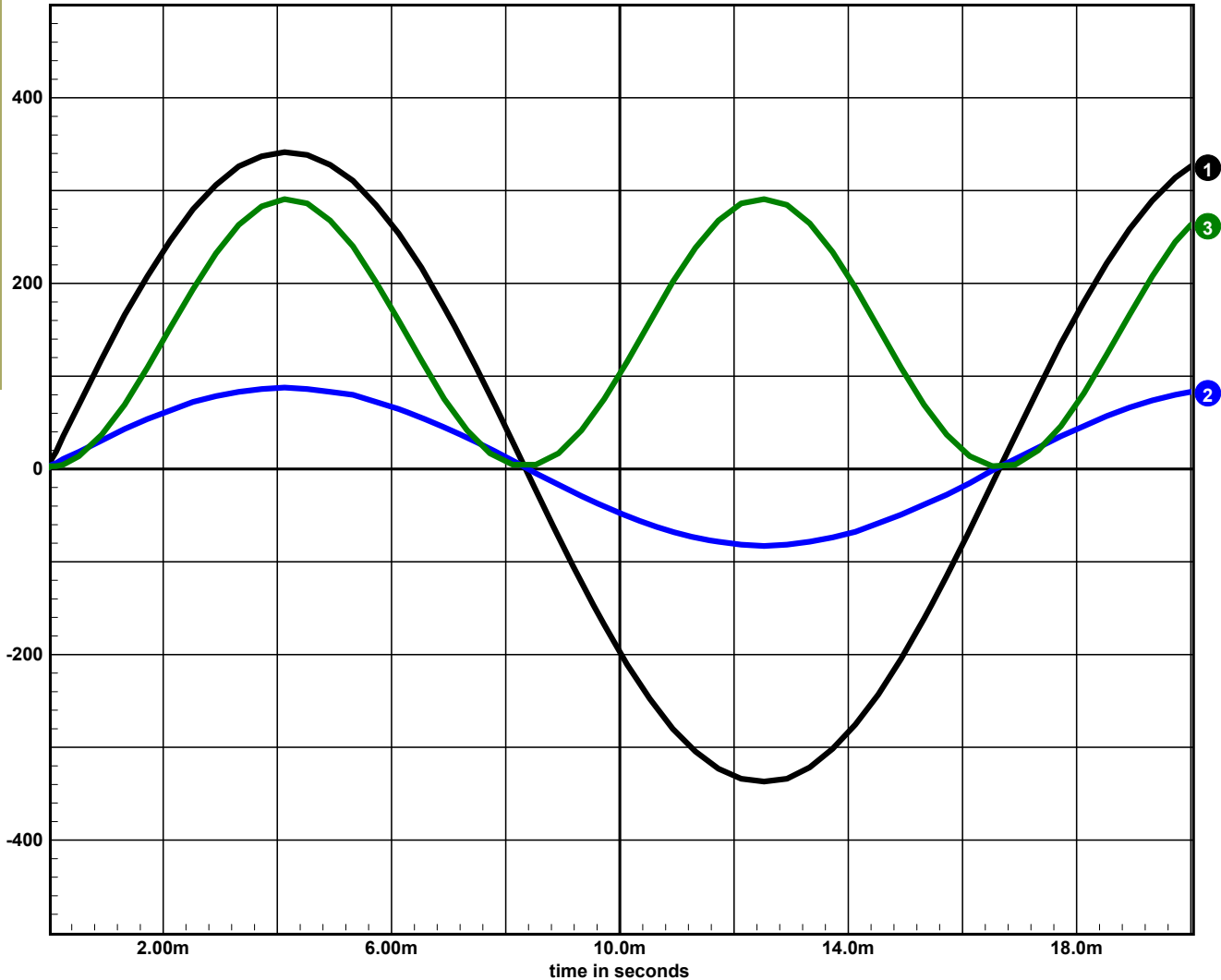
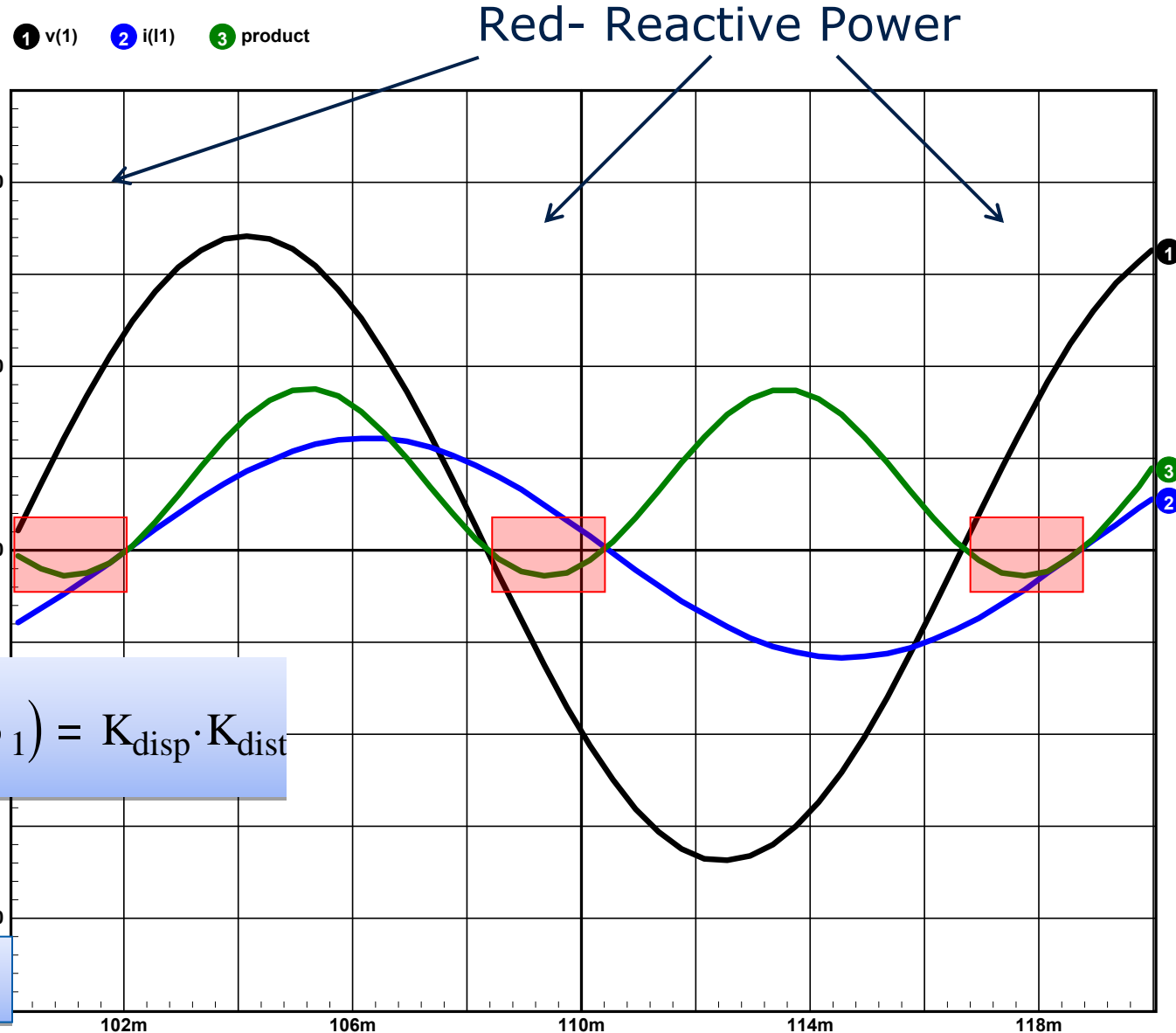
# Sinusoidal $v(t)$ & Sinusoidal $i(t)$ with $PF < 1$

Reactive power  
Oscillates  
between  
Source and  
reactive part  
of load  
(cap or inductor)  
Current  
Phase Shift  
Cap ( $0 < \Phi < 90$ )  
Ind ( $-90 < \Phi < 0$ )




$$P.F = \frac{I_{rms1}}{I_{rms}} \cdot \cos(\theta_1 - \phi_1) = K_{disp} \cdot K_{dist}$$

$$K_{dist} = \frac{I_{rms1}}{I_{rms}} = 1$$

$$P.F = K_{disp}$$

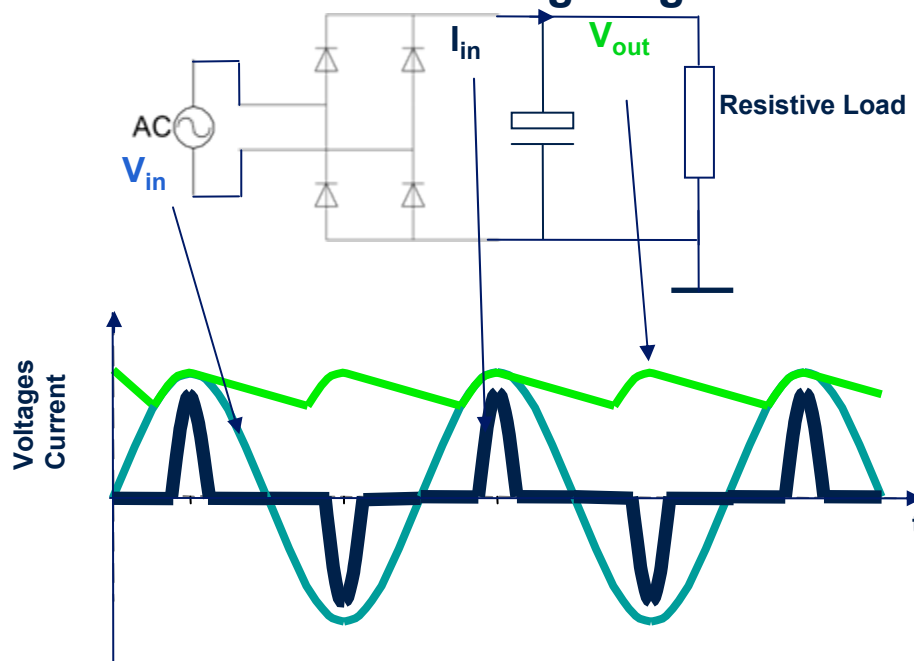- ☹ **The input current in a system with diode rectifier followed by a capacitor is nonsinusoidal: This is observed in Lighting Solutions**





- **Problems:**

- a large harmonic component in the distorted input current leads to an increasing pollution of the mains voltages
- the amount of reactive power is dramatically increased  
(a 100W TV set consumes 90W reactive power => The input power is only partly transferred to the output)

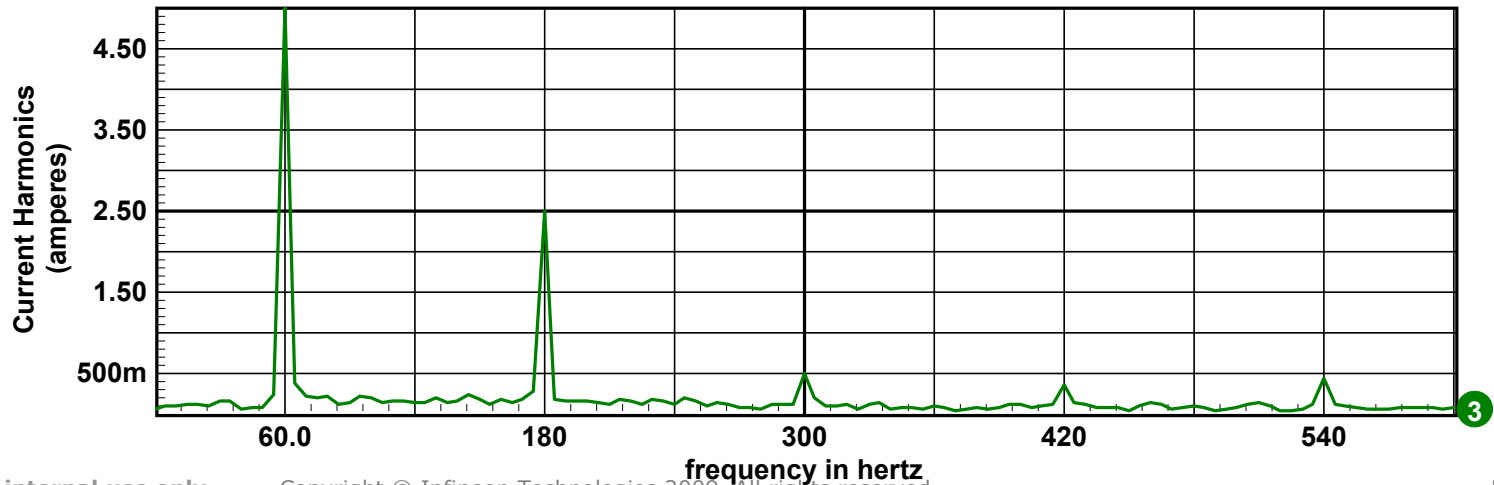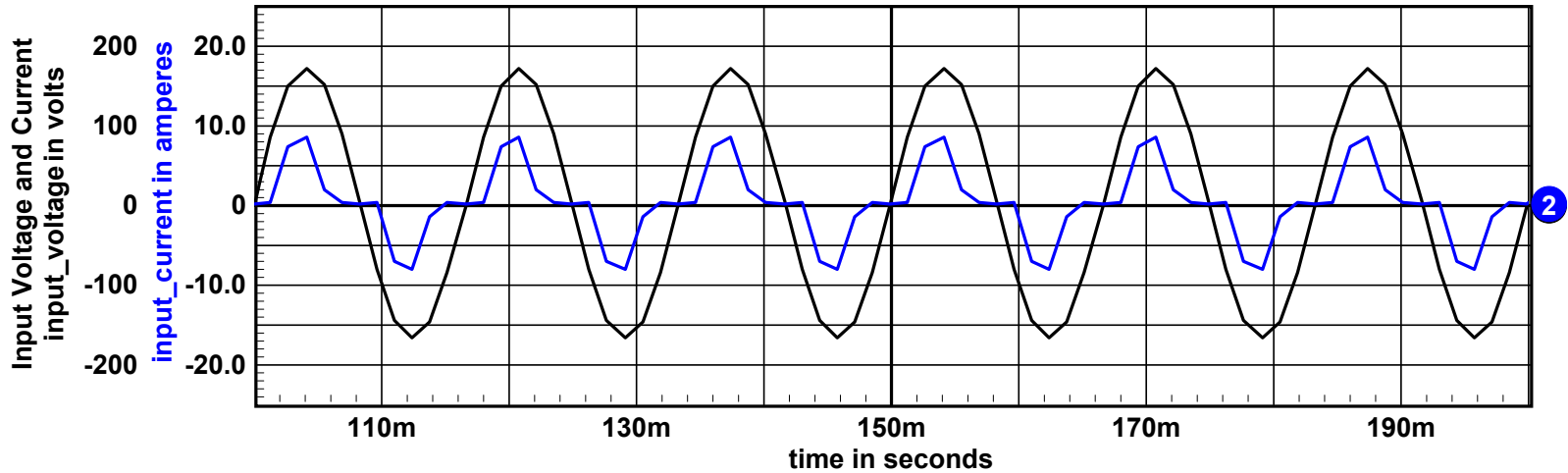
# Harmonic Content

① input\_voltage    ② input\_current    ③ harmonic\_content


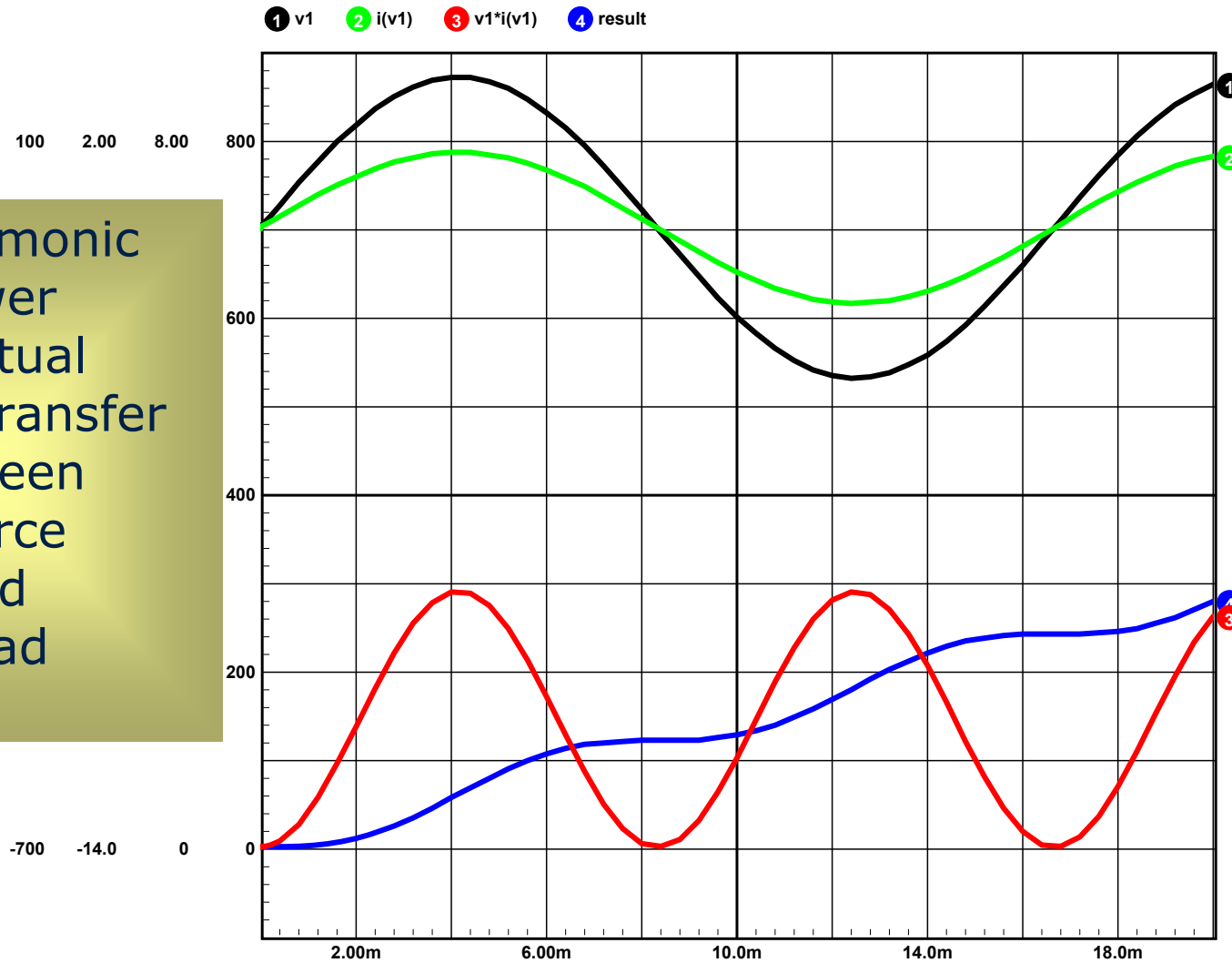
# 1<sup>st</sup> Harmonic Power

1<sup>rd</sup> Harmonic Power  
Is actual  
Power Transfer  
between  
Source  
and  
Load




Total energy transfer is positive all the time.

# 3<sup>rd</sup> Harmonic Power

3<sup>rd</sup> Harmonic Power Oscillates between Source and Load

Apparent power only!!!

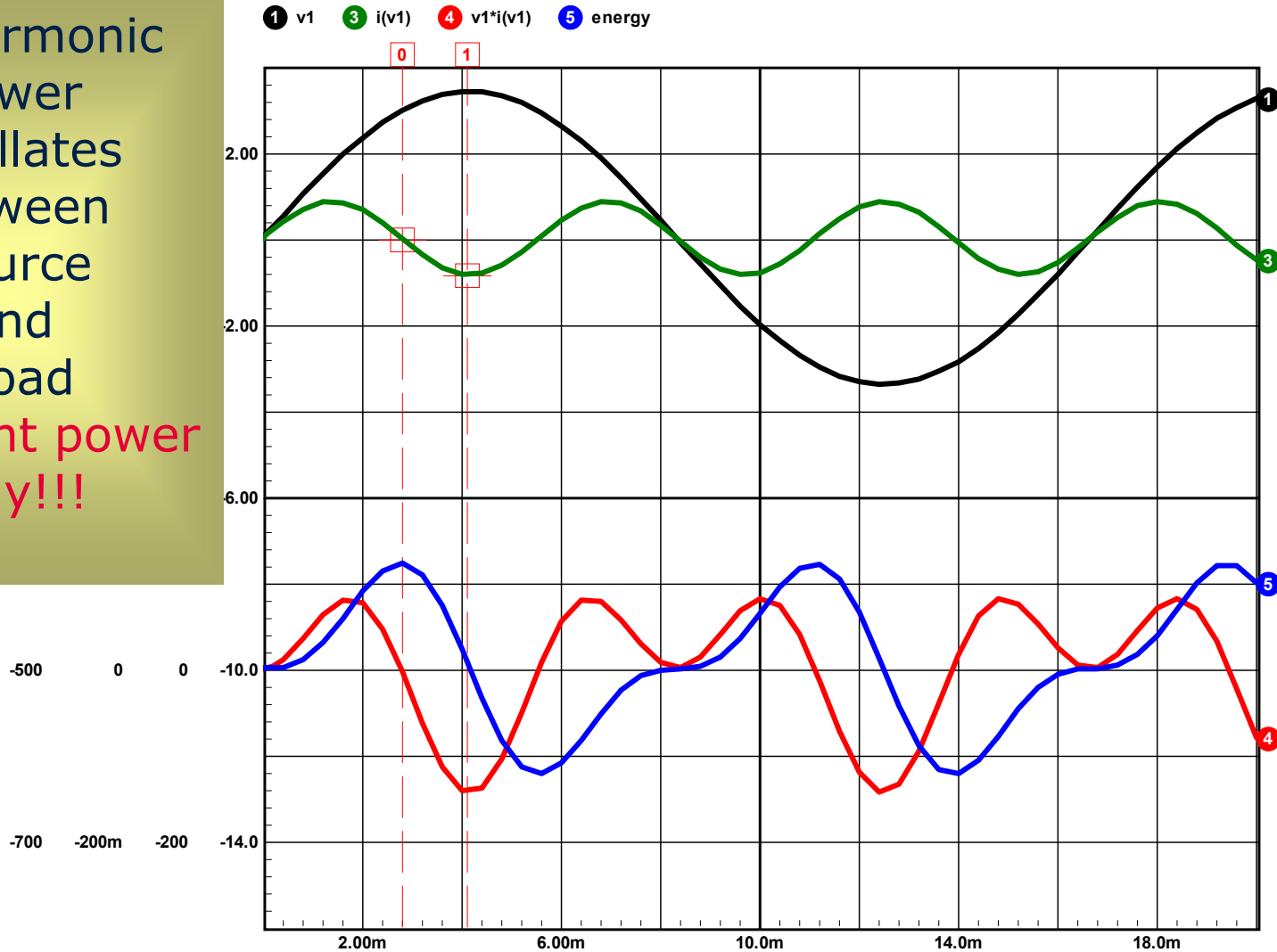

Total energy transfer after each half period is equal zero "0"

# Power Factor Formula for Non-Linear Loads:

- Power Factor Formula:


$$P \cdot F = \frac{I_{rms1}}{I_{rms}} \cdot \cos(\theta_1 - \phi_1) = K_{disp} \cdot K_{dist}$$

- $V(t)$  and  $i(t)$  fundamental components are in phase;

$$\cos(\theta_1 - \phi_1) = K_{disp} = 1$$


- $P \cdot F = K_{dist} = \frac{I_{rms1}}{I_{rms}} < 1$

# AC-DC conversion with and without PFC

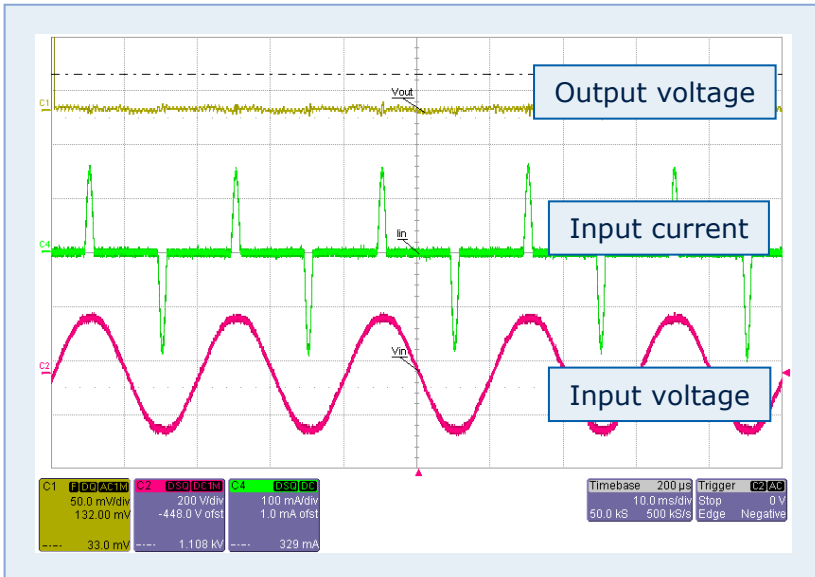

Without Power Factor Correction

**Power factor: 0.43**

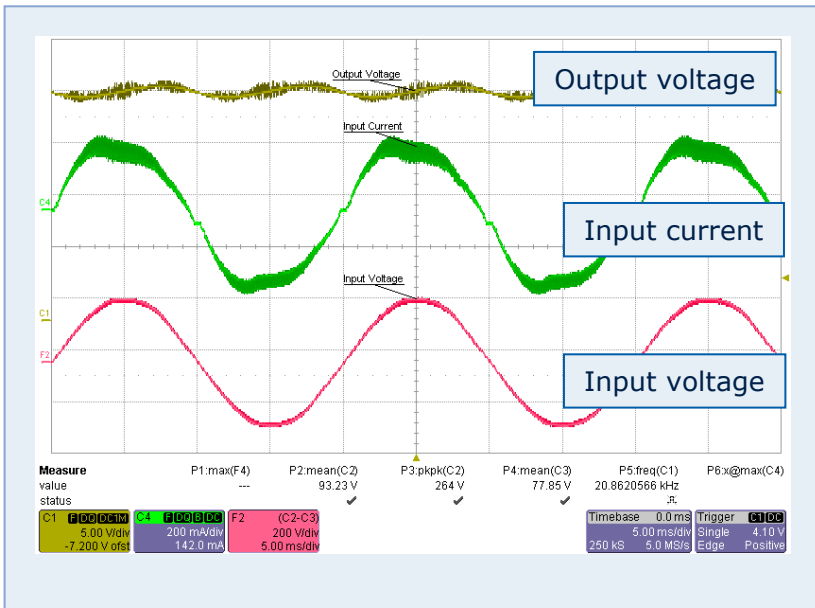

**With** Power Factor Correction

**Power factor: >0.90 !**

Power Factor basics

Definition of Power factor

PF for various loads

Total Harmonic Distortion

PF correction methods

ICL8001G: High PFC Dimmable LED Driver

# Total Harmonic Distortion

- A frequently-used measure of harmonic levels is total harmonic distortion (or distortion factor), which is the ratio of the rms value of the harmonics (above fundamental) to the rms value of the fundamental, times 100%, or:

$$\text{THD}_I = \frac{I_{\text{rms}}(\text{Distorted})}{I_{\text{rms1}}} \times 100$$

$I_{\text{rms}}(\text{Distorted})$  is the sum of all the harmonics other than the fundamental.

$$I_{\text{rms}}(\text{Distorted}) = \sqrt{I_{\text{rms}}^2 - I_{\text{rms1}}^2}$$

$$\text{THD}_I = \sqrt{\left(\frac{I_{\text{rms}}}{I_{\text{rms1}}}\right)^2 - 1} \times 100$$


$$\text{PF} = \frac{1}{\sqrt{1 + \frac{\text{THD}_I}{100}}}$$

# Total Harmonic Distortion

- Incorporating these two assumptions

*( $P_{avg} \approx P1_{avg}$  and  $V_{rms} \approx V1_{rms}$ )*

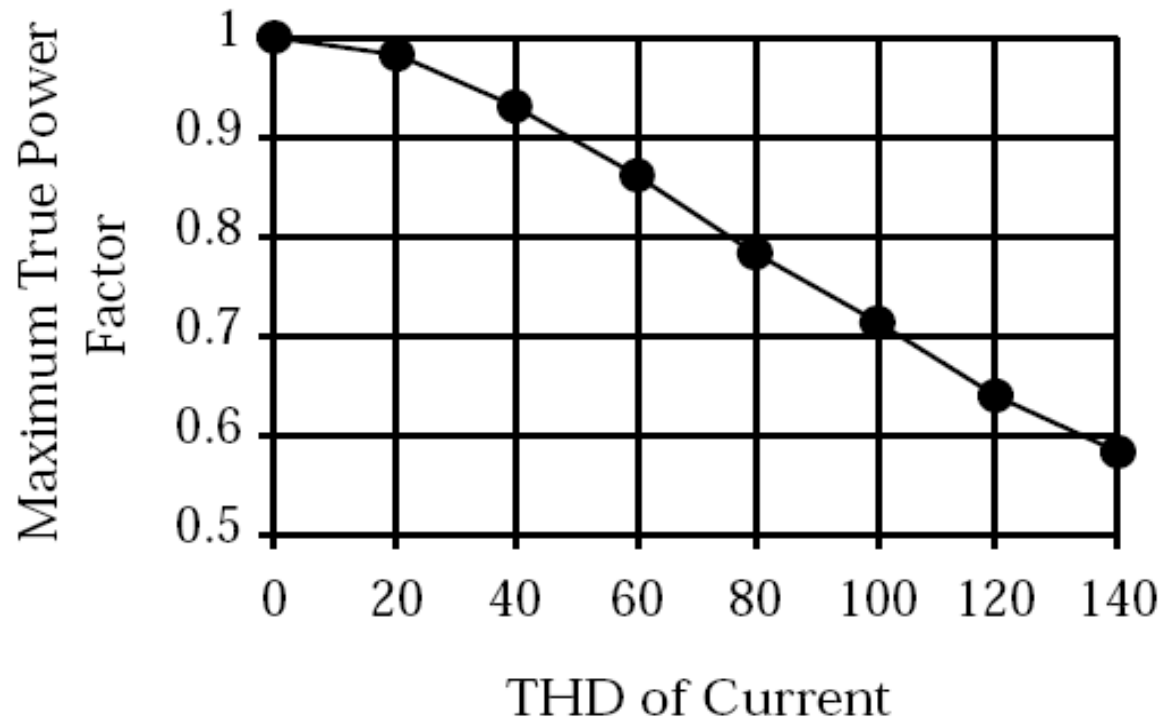the following approximate form for Power Factor:



Power Factor basics

Definition of Power factor

PF for various loads

Total Harmonic Distortion

PF correction methods

ICL8001G: High PFC Dimmable LED Driver


## Passive Solution

by iron core choke

Characteristics:

Pros: rugged, supports EMI, cheap

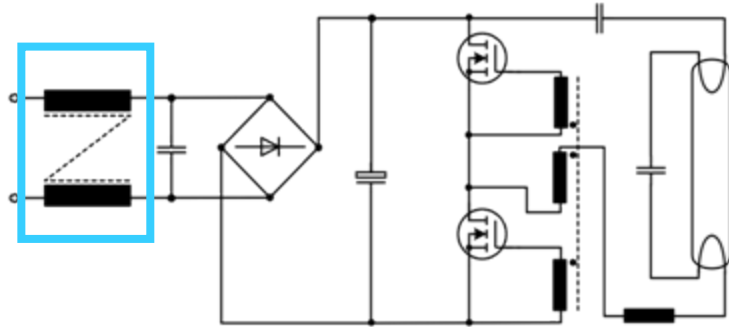Contras: heavy, big, tends to humming  
output voltage dependent on load




## Active Solution

by ferrite/powder core choke, diode,  
MOSFET, control IC

Characteristics:


Pros: light, effective, output voltage stable  
allows wide input voltage range

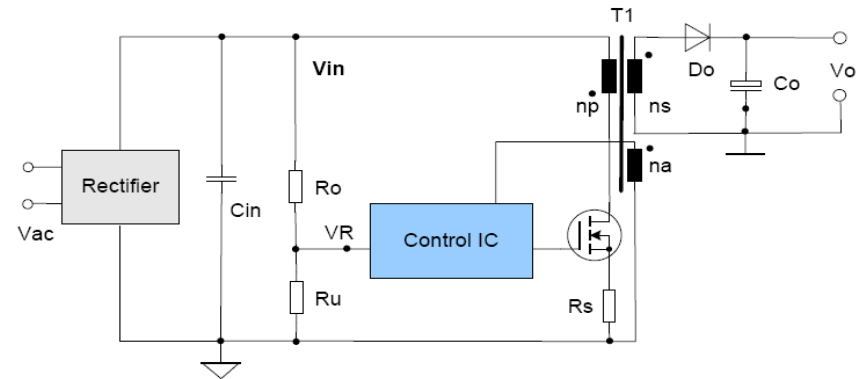Contras: additional components but costs partially  
compensated in remaining system


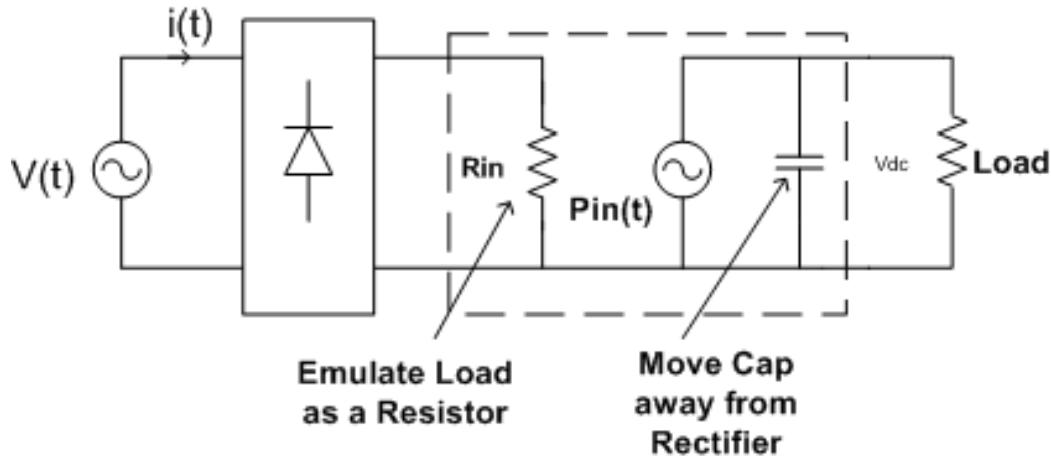
# Active Power Factor Correction Concept

- Emulate Load after bridge rectifier as a lossless resistor.



- Output ripple is twice the line frequency.

- Conversion ratio = 
$$\frac{V_{dc}}{V_{in} \cdot |\sin \omega t|}$$

- Control is needed for  $R_{in} = V_{in}^2 / P_{in}$  to provide required output power.


# Active Power Factor Correction Concept

- Slow control loop. Cross-over frequency should be about 20Hz at high line input voltage.
- Input Voltage Feed-forward is required to provide constant output Regulation. The input voltage feed-forward must be constant during each half cycle.
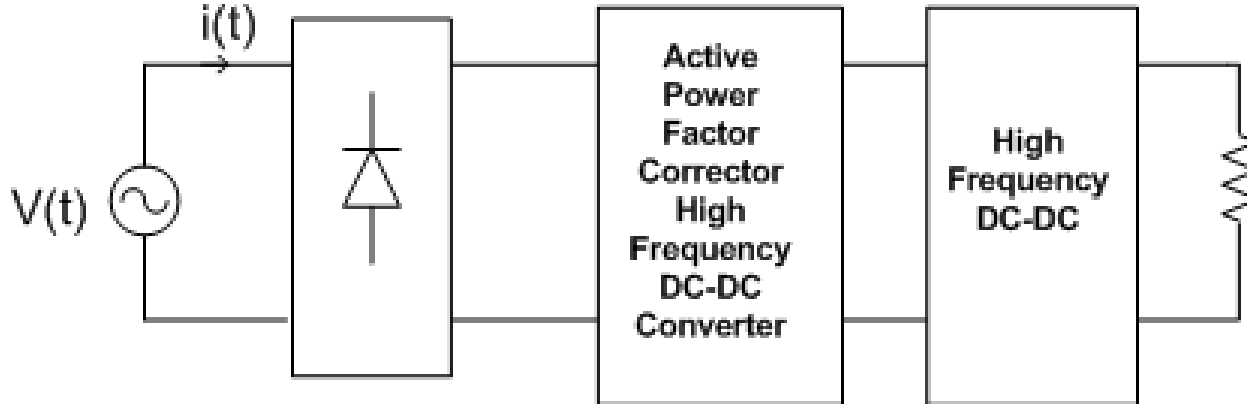
# Active Power Factor: Two Stage Method


- Two Stage Method

- Tight Output Voltage Regulation at load is provided by second stage.



- Boost most commonly used. CRM for  $P_o < 250$  watts; CCM Average current mode control for  $P_o > 250$  watts


## ■ Single Stage Method

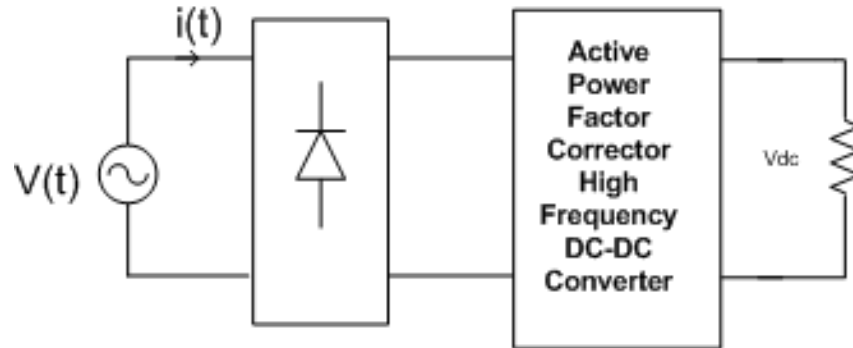

- ❑ Output Voltage Regulation at load is not tight.
- ❑ High output ripple (second harmonic) at load. Used in applications such as LED lighting in which high output ripple voltage is inconsequential.
- ❑ CRM Flyback (Buck-Boost) most commonly used.
- ❑ Coupled inductor provides galvanic Isolation for safety is provided.

# Control Methods for Boost-Converter
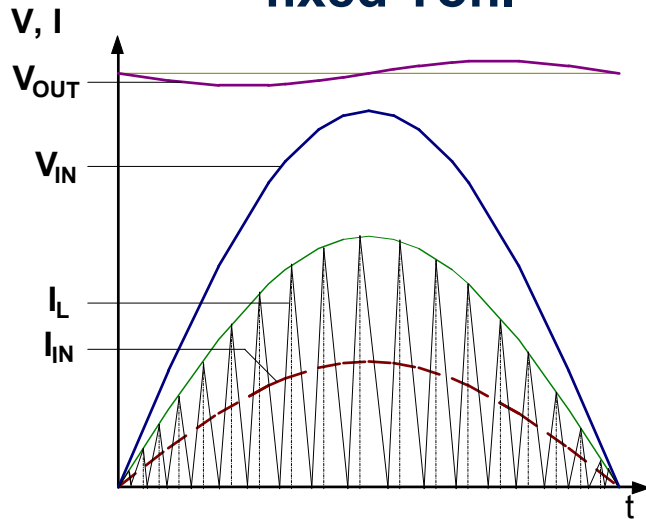
## Critical Conduction Mode CRM Variable frequency fixed $T_{on}$ .



### Characteristics:


Pro

no reverse recovery losses of diode  
simple control method

Contra

difficult smoothing of peak currents  
at light load
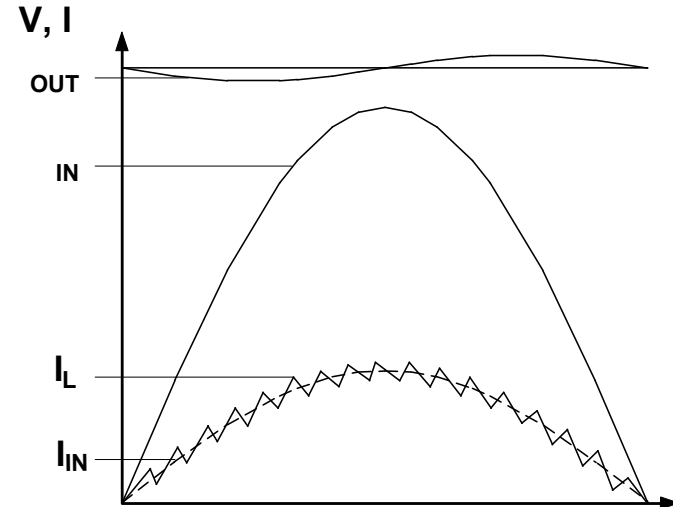
## Continuous Current Mode CCM usually constant frequency



### Characteristics:

Pro


easy smoothing of peak currents  
stable operation at light load

Contra

reverse recovery losses of diode  
complex control method


# Active Power Factor Correction: PFC Flyback Converter features

Advantages	Disadvantages
<ul style="list-style-type: none"> <li>- Is inherently a Power Factor Corrector when operated in DCM. Simple hysteretic fixed ton control.</li> </ul>	<ul style="list-style-type: none"> <li>- High Voltage Stress on MOSFET and diode.</li> </ul>
<ul style="list-style-type: none"> <li>- Coupled Inductor provides galvanic isolation for safety.</li> </ul>	<ul style="list-style-type: none"> <li>- Filtering for EMI due to switching input current. However, this problem is reduced by QR operation.</li> </ul>
<ul style="list-style-type: none"> <li>- Inherent Current limiting.</li> </ul>	
<ul style="list-style-type: none"> <li>- Low Cost: Few Components, single stage . Can Buck &amp; Boost.</li> </ul>	

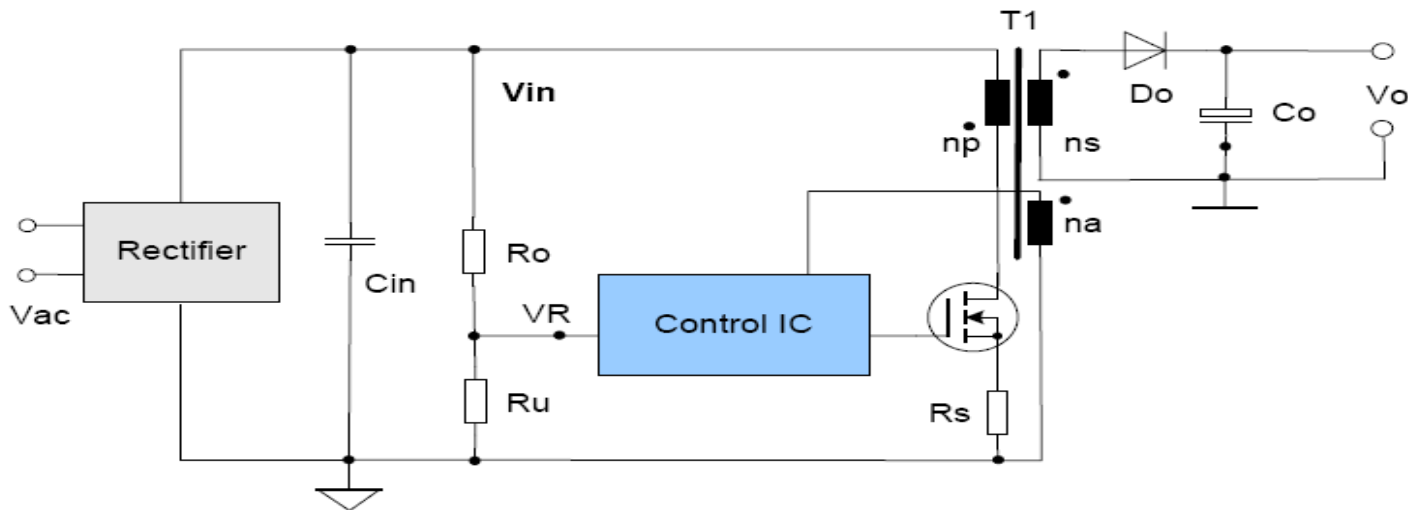
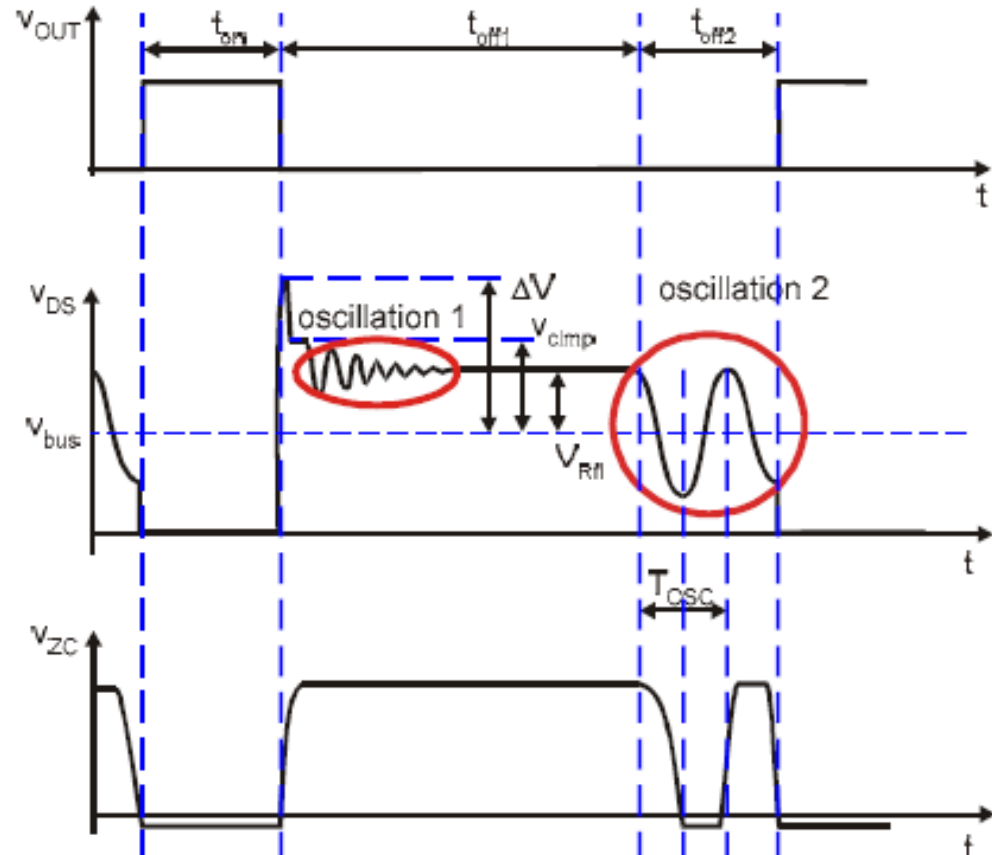
# Flyback with QR operation

- Flyback can be implemented with FF or QR. QR offers the following advantages:
- High efficiency due to zero voltage switching.
- Reduced EMI noise.



# Agenda Overview



Power Factor basics

Definition of Power factor

PF for various loads

Total Harmonic Distortion

PF correction methods

ICL8001G: High PFC Dimmable LED Driver

## LEDs AND POWER FACTOR CORRECTION.



### ■ Requirements for LED solutions:



- Appears to the source as a resistive load
- Meets regulatory, market and safety requirements
- Control to provide required output power.
- LOW COST (Let us not Forget):
  - Solution: Single Stage Flyback.
    - Very few components --primary side control results in as few as 20 components.
    - Has inherent current limiting. No added circuitry for protection.
    - Simple low cost hysteretic control can be used.
    - Inherent very high PF.
    - Full galvanic isolation

# ICL8001G: Single Stage LED Driver
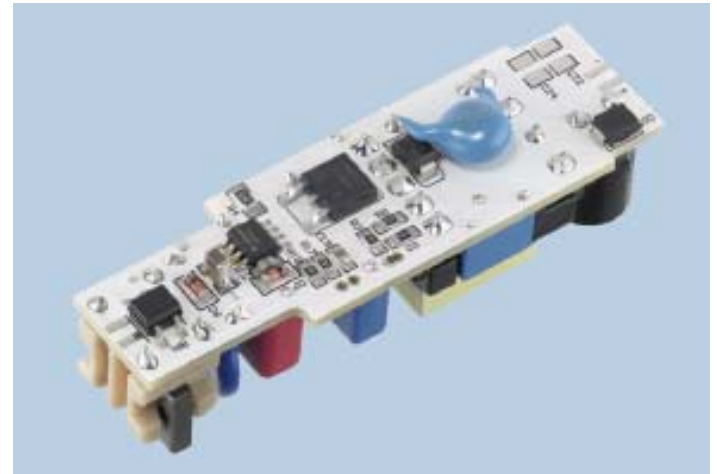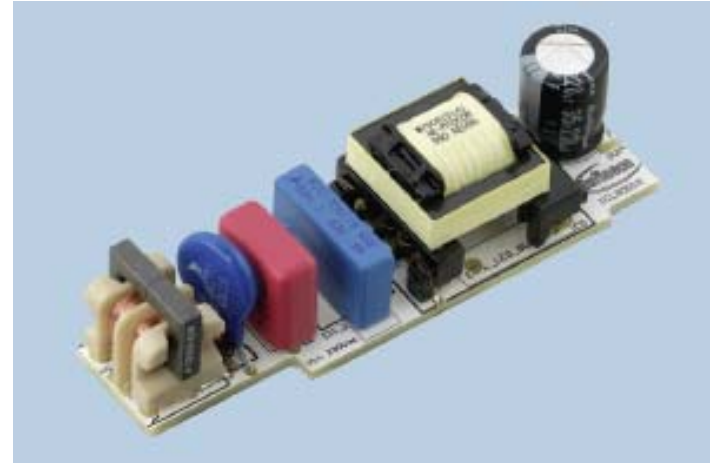
## ICL 8001G Performance

- vs standard PFC controller -

- Precise PWM generation
- Propagation delay correction
  - Fold back correction
  - Start Up Cell
- Programmable Protection




# ICL8001G: Single Stage LED Driver

## LED Bulb QR Flyback Driver with ICL8001G for

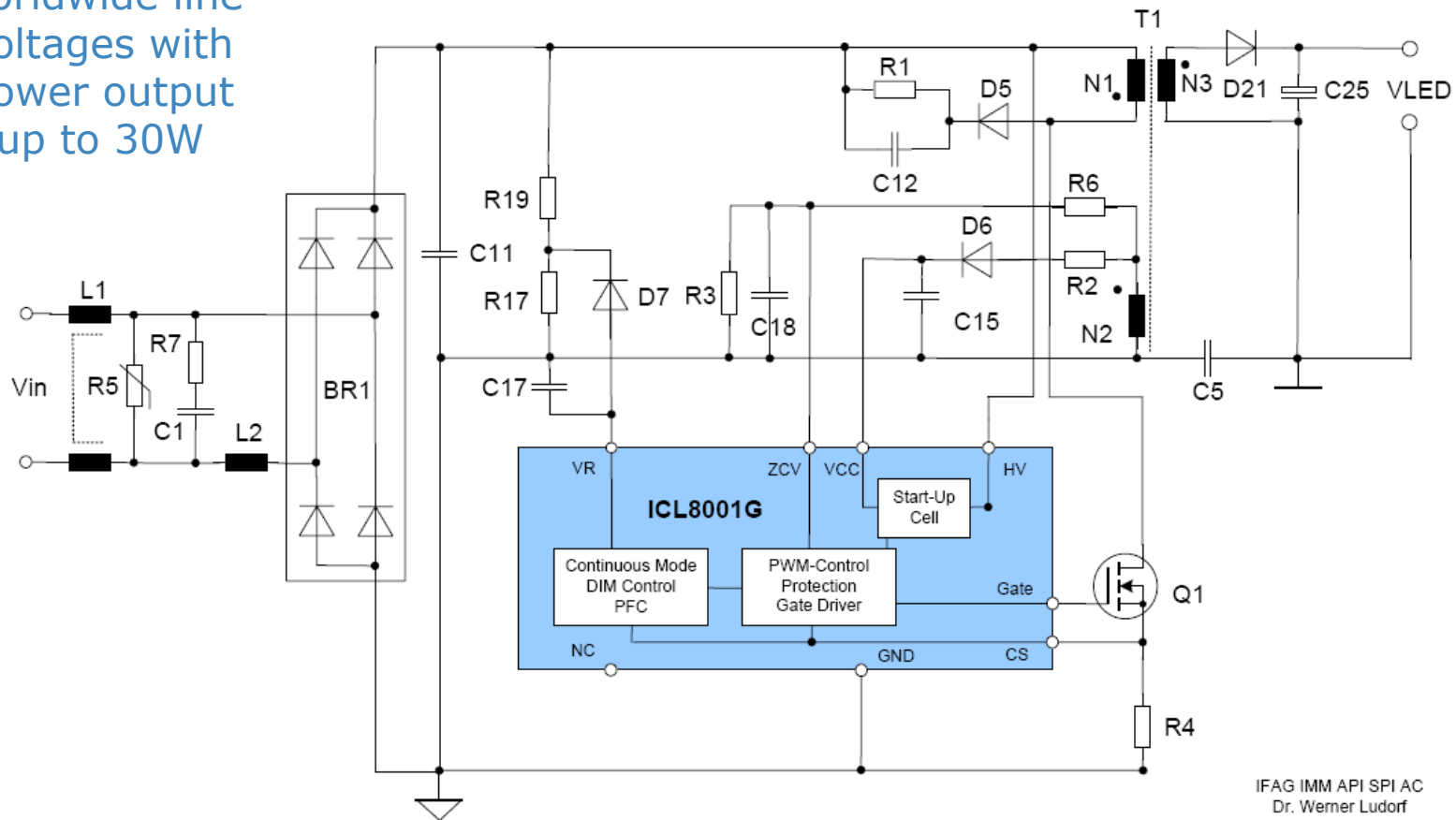
### Phase Cut Dimming & PFC using Primary Control

Supports worldwide line voltages with power output up to 30W




IFAG IMM API SPI AC  
Dr. Werner Ludorf

# PFC performance

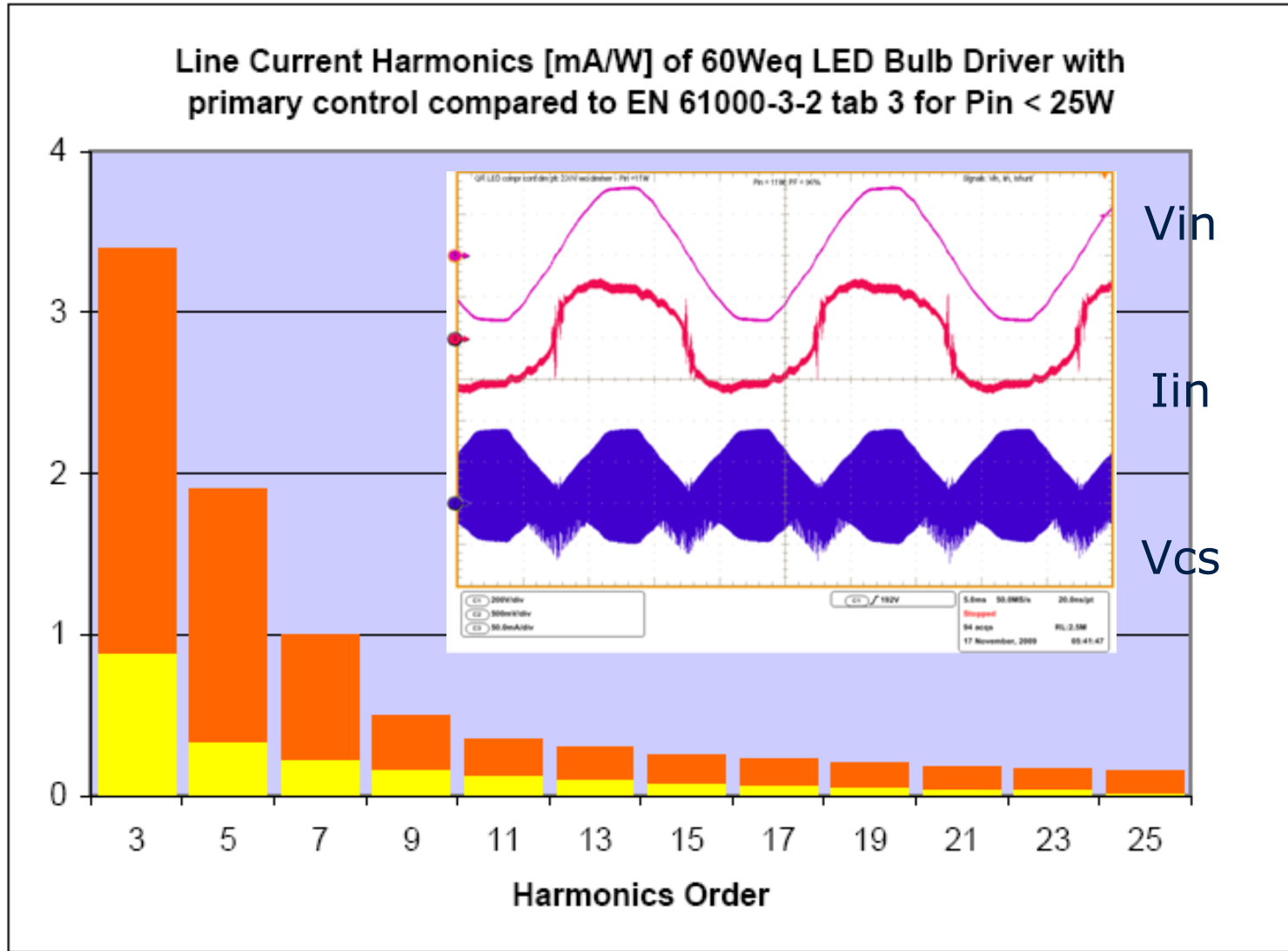


# Phase Cut Dimming – Leading Edge

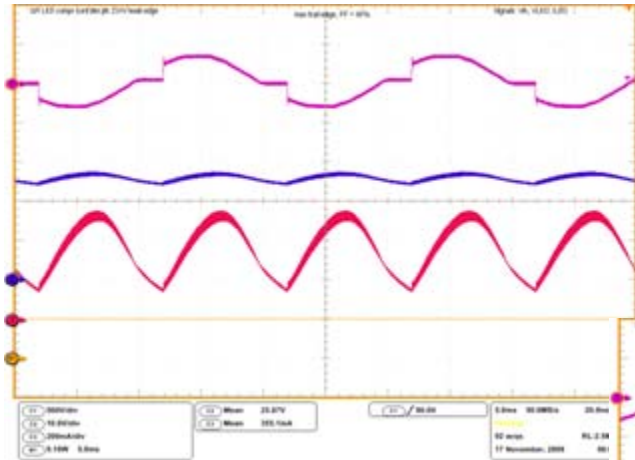

Maximum Dimming-Level


- PFC function as ideal precondition for stable leading edge dimmer operation
- Oscillations caused by interaction of EMI filter with leading edge dimmer are depending on EMI filter design applied

Medium Dimming-Level

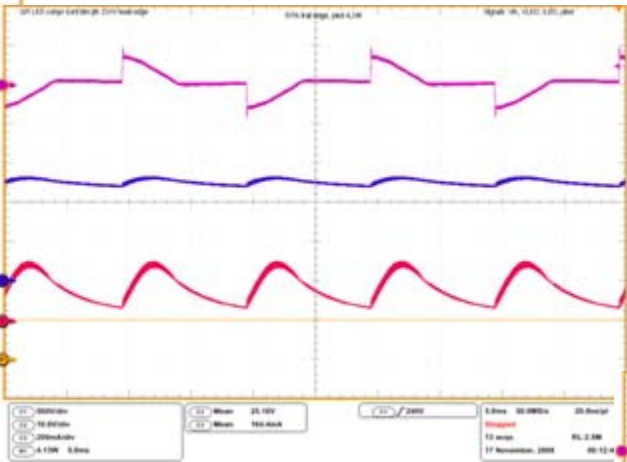


Vin  
Vout  
Iout

Minimum Dimming-Level

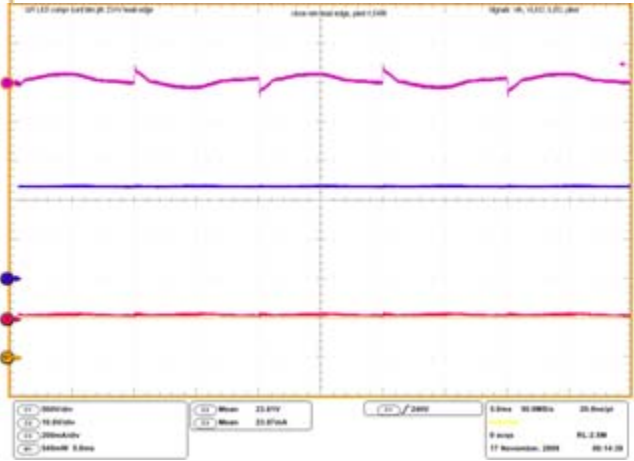


Reference Dimmer : Ehmann Lumeo Domus 1060 60-300W

# Phase Cut Dimming – Trailing Edge

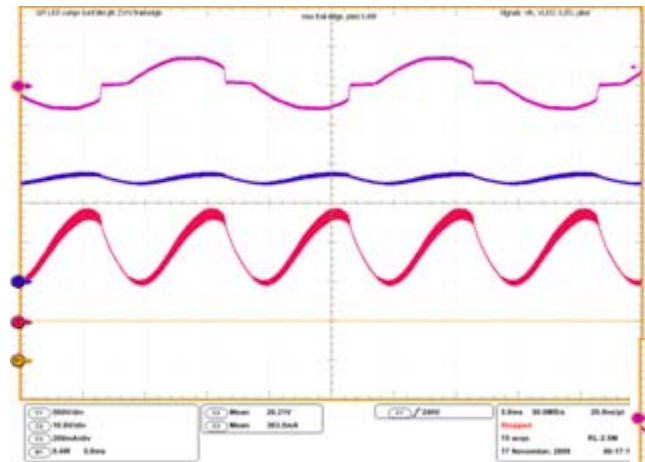


Maximum Dimming-Level

Medium Dimming-Level

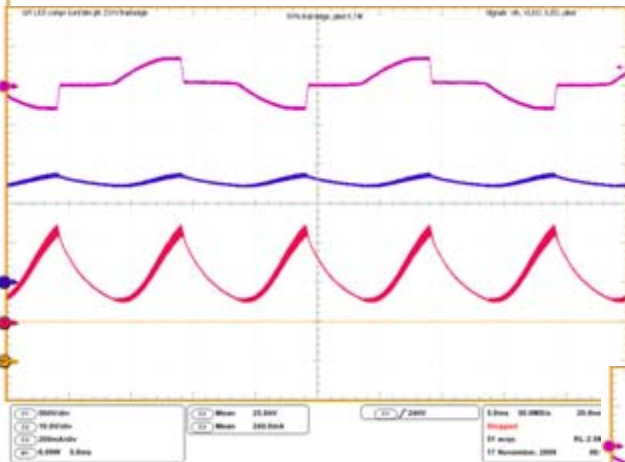

Vin  
Vout  
Iout

Minimum Dimming-Level

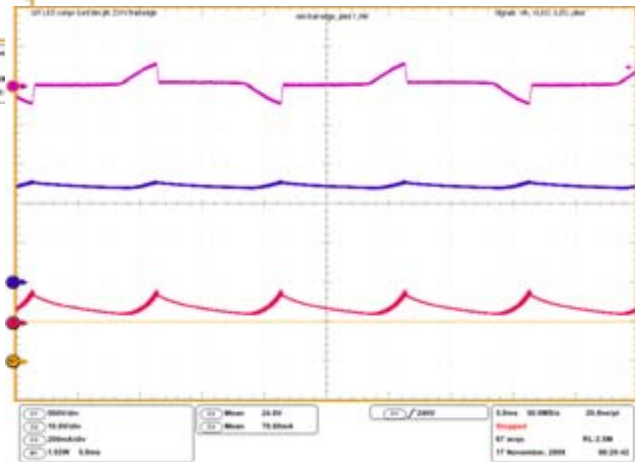

Reference Dimmer : Ehmman Lumeo Domus 4660 20-315W

# LED Bulb Driver with ICL8001G Feature Summary




- Best in class BOM cost with 30% material cost reduction
- Isolated Driver output for efficient thermal management
- High quasiresonant ( QR ) flyback driver efficiency up to 90%
- High power factor  $PF > 98\%$  adjustable
- Phase cut controlled continuous LED current dimming
- Primary side output power control
- Small formfactor fits E27 bulb
- Cycle by cycle current limitation
- Output short circuit and output over voltage protection
- Over temperature detection

# Backup material

- Additional PFC corrected LED solutions from Infineon.
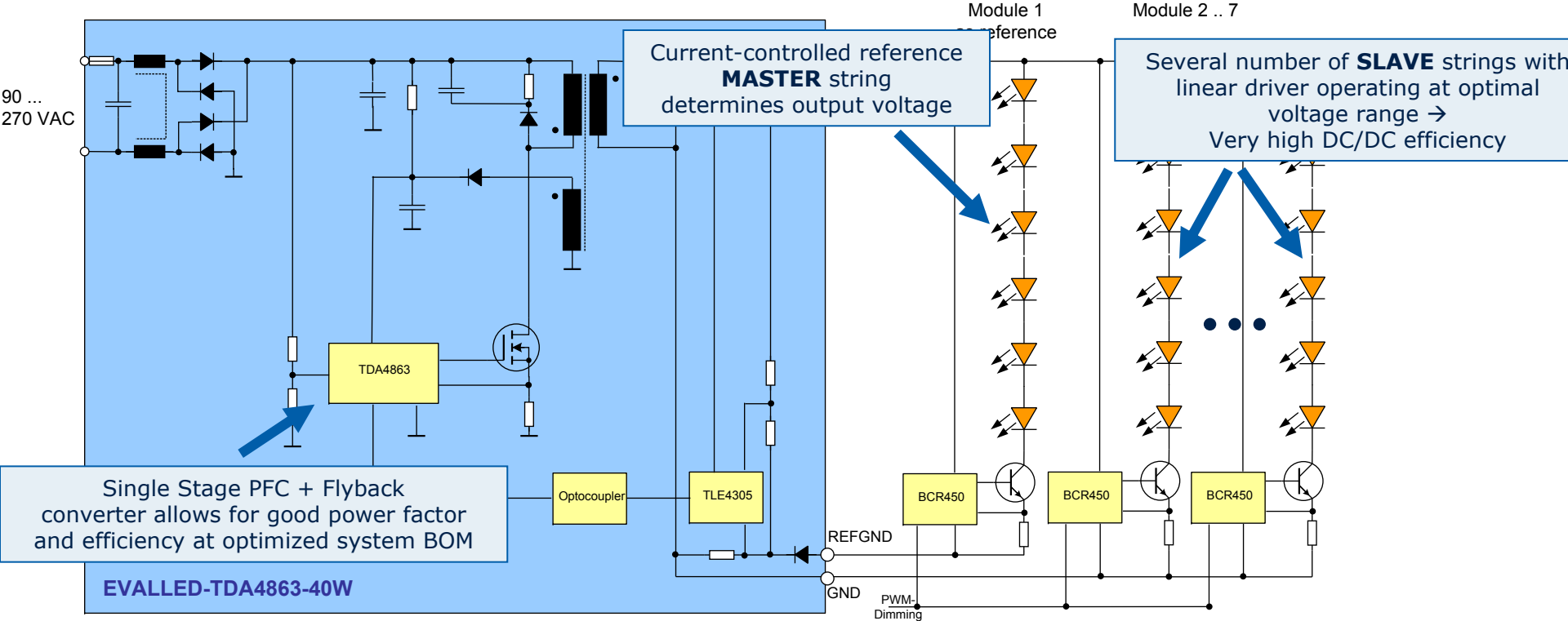
# Single Stage PFC with Fly-back combined with linear drivers on secondary side




## Optimized System Solution:


Combination of single-stage PFC + Flyback AC/DC converter, constant current control and linear drivers allows

- high power factor,
- high efficiency and
- no EMI on secondary side
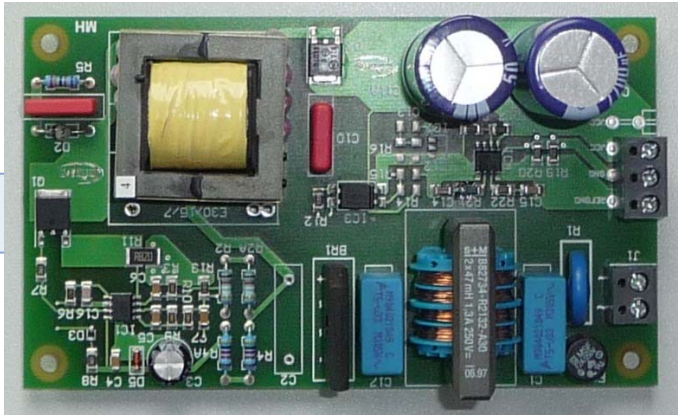
# Off-Line LED Driver Solution 40W Single Stage Evaluation Board




Order Code **EVAL-LED-TDA4863G-40W**

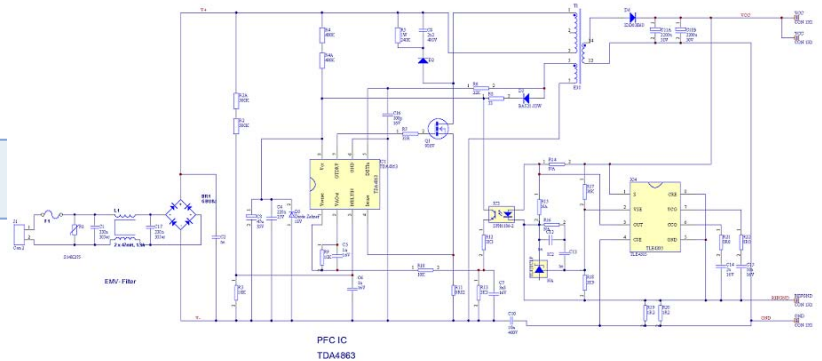

- TDA4863 Flyback controller & PFC in a single stage topology
- TLE4305 CV CC Feedback
- Optimised for low cost multi LED string system with BCR450 linear current regulators
- Scalable and low cost BOM

- 40W Output: Input 190-270V AC
- 20W Output: Universal Input
- Variable, Stable Output (15V-25V)
- High Efficiency ~88% (AC to LED)
- High Power Factor >0.9
- **Order Code EVAL-LED-TDA4863G-40W**
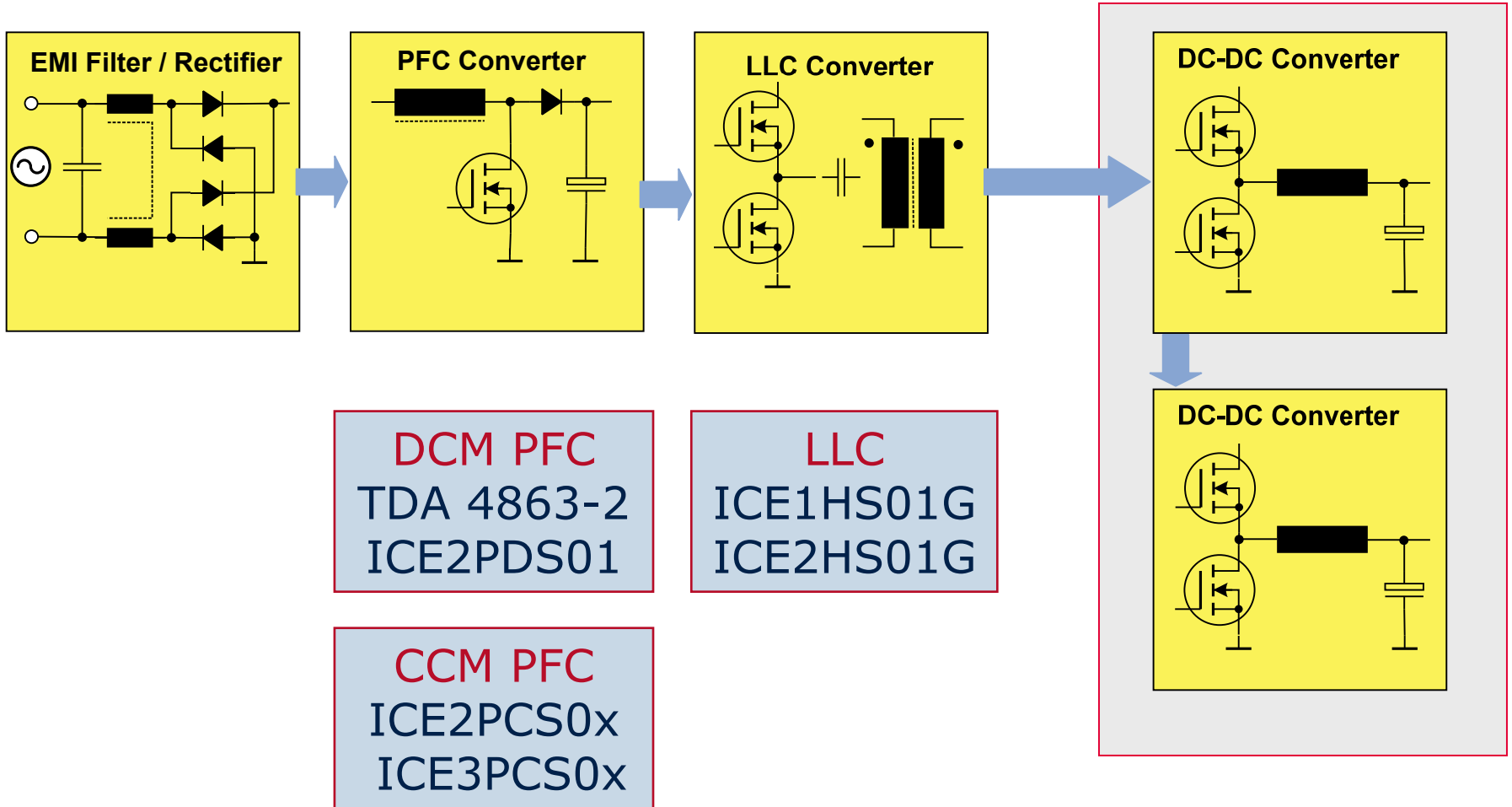
# High Power Lighting Power Supply Architecture PFC+LLC [+DC-DC]





**We commit.**  
**We innovate.**  
**We partner.**  
**We create value.**



Never stop thinking